

KABARAK



UNIVERSITY

UNIVERSITY EXAMINATIONS
MAIN CAMPUS

SECOND SEMESTER, 2017/2018 ACADEMIC YEAR

EXAMINATION FOR THE DEGREE OF BACHELOR OF SCIENCE IN
TELECOMMUNICATIONS AND BACHELOR OF EDUCATION
SCIENCE

PHYS 120 BASIC ELECTRONICS

STREAM: PARTIME

TIME: 1.00-3.00P.M

EXAMINATION SESSION: APRIL 2018

DATE: 14/04/2018

QUESTION 1 (30 MARKS)

- a) Give the symbols for npn and pnp transistors 2 marks
- b) Differentiate between conductors, insulators and semiconductors on the basis of bandgap. 6 marks
- c) The circuit shown in **Figure 1.1** is to be designed such that $I_{CQ} = 0.9 \text{ mA}$ and $V_{CEQ} = 2.5 \text{ V}$ for the case when $R_E = 1 \text{ k}\Omega$. Assume $V_{BE}(\text{on}) = 0.7 \text{ V}$ and $\beta = 80$. Find R_B and R_C . 6 marks

As members of Kabarak University family, we purpose at all times and in all places, to set apart in one's heart Jesus as Lord. (1 Peter 3:15)

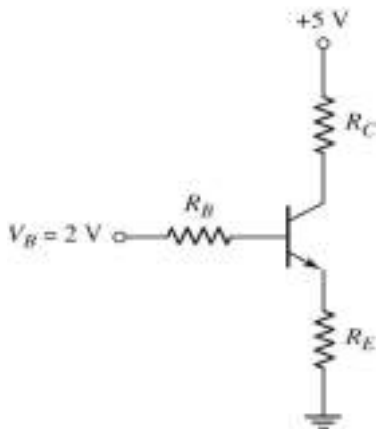



Fig. 1.1

d) Explain the difference between drift and diffusion mechanisms in semiconductors

3 mark

e) Draw the output voltage waveforms for the circuit in figure 1.2

2 marks

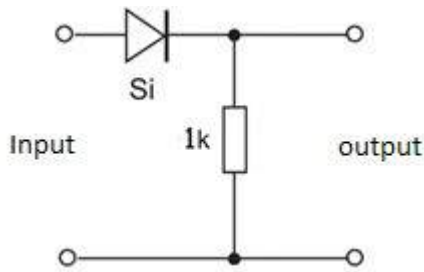

f) Discuss the similarities and differences between JFET and MOSFET with regard to their construction and applications.

4 marks

g) **Fig. 1.3 (a)** is a clipper circuits. Sketch on Figure 1.3 (b) the output voltage, V_O if the input signal, V_i is a 12V peak-to-peak square wave. Assume that $V_{th} = 0.6V$.

3 marks

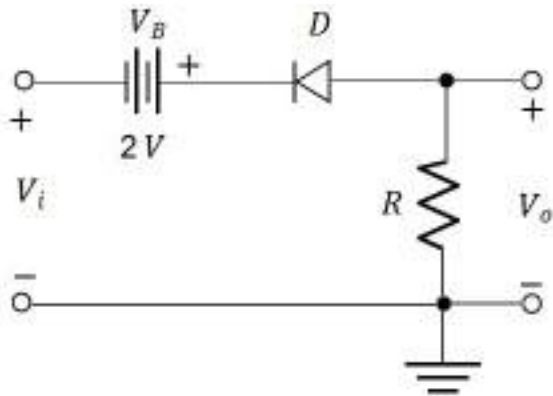


Fig. 1.3 (a)


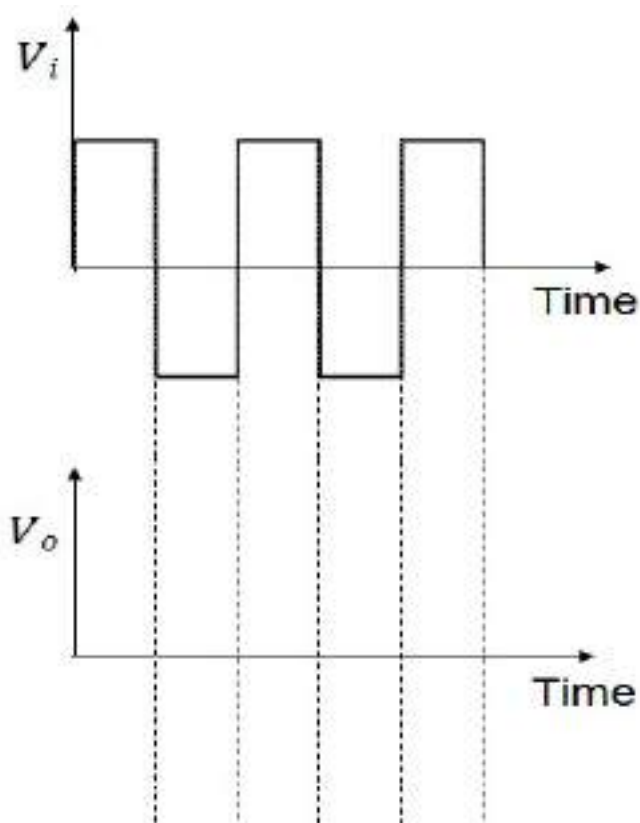


Figure 1.3 (b)

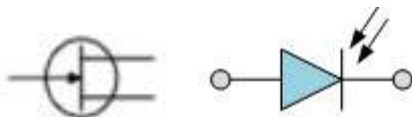h) Give the name and role of devices represented by the following two symbols. 4 marks



QUESTION 2 (20 MARKS)

- a) Describe how Current-Voltage characteristics of a Zener diode can be determined in the laboratory? 10 marks
- b) Discuss potential divide method of biasing clearly proving its superiority over other methods. 10 marks

QUESTION 3 (20 MARKS)

- a) The transistor used in circuit (Figure 3.1(a)) has the characteristics shown on the graph (Figure 3.1(b)).

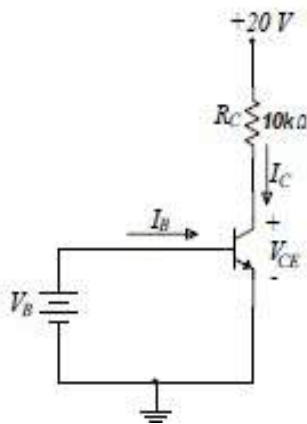


Figure 3 (a)

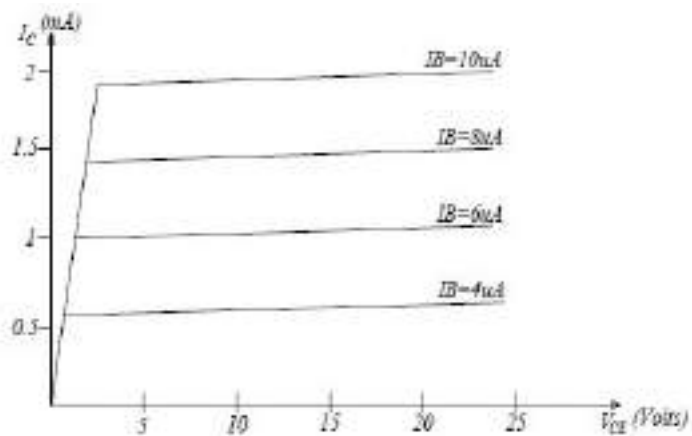


Figure 3 (b)

- i. Copy the graph and draw the loadline. 5 marks
- ii. On the loadline, locate the Q-point for $I_B = 6\mu A$ 2 marks
- iii. Estimate the value of the transistor β . 2 marks
- b) Illustrate graphically the three operating modes of BJT. Explain the biasing conditions of the B-E junction and B-C junction of the BJT for operation in each mode. 8 marks
- c) Label parts marked A, B, and C of an npn transistor given below (Figure 3.2). 3 marks

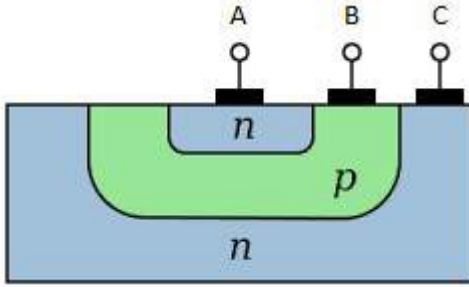


Figure 3.2

QUESTION 4 (20 MARKS)

a) Refer to Figure 4.1 .

- i) Show that the gain can be calculated from: $A_v = 1 + \frac{R_f}{R_1}$. 4 marks
- ii) Determine the voltage gain for the circuit, with $R_f = 100\text{K}\Omega$ and $R_1 = 10\text{K}\Omega$. 2 marks

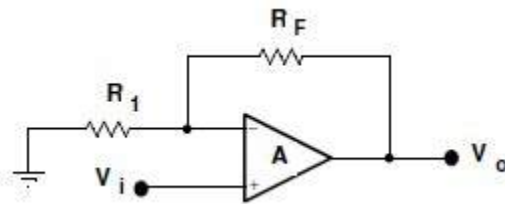


Figure 4.1

- b) The circuit of a **Single Stage Common Source N-channel JFET** amplifier using self bias is shown in fig. 4.2. Explain the purpose of each component Used. 7 marks

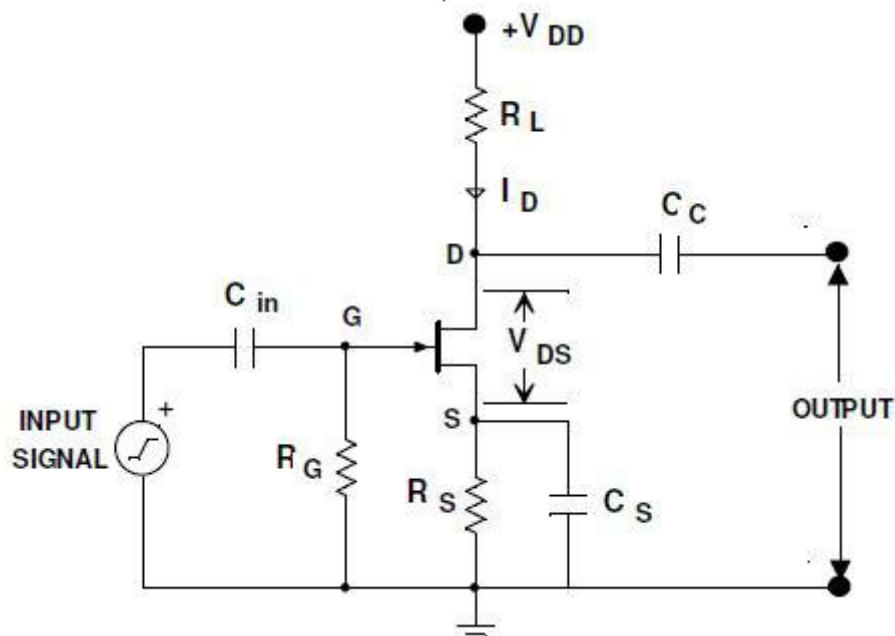


Figure 4.3

- c) With suitable diagrams and/or a graph, explain how the gate voltage controls the output. 7 marks

QUESTION 5 (20 MARKS)

- a) A Zener diode is connected in a voltage regulator circuit as shown in **Fig. 5.1**. It is given that $V_{PS} = 20\text{V}$, the Zener voltage, $V_Z = 10\text{V}$, $R_i = 222\ \Omega$ and $P_{Z(\max)} = 400\text{ mW}$.
- Determine the values of I_L , I_Z and I_I if $R_L = 380\ \Omega$. 6 marks
 - Determine the value of R_L that will establish $P_{Z(\max)} = 400\text{ mW}$ in the diode. 2 marks

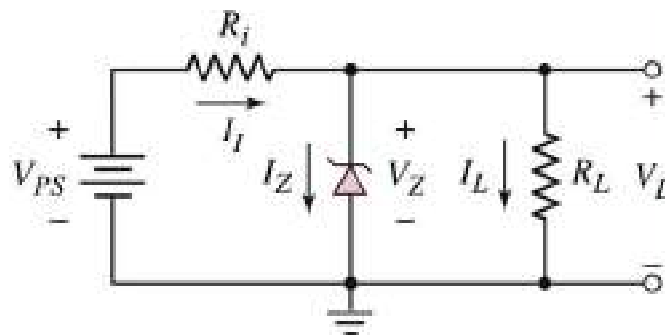


Figure 5.1

- b) The following values are given as design data for the *BJT* configuration shown in **Figure 5.2**: $V_{CC} = 12\text{V}$, $V_{BB} = 5\text{V}$, $I_C = 15.5\text{ mA}$, $V_{CE} = 5.8\text{V}$, $I_B = 100\ \mu\text{A}$ and $V_{BE(\text{on})} = 0.7\text{V}$.

As members of Kabarak University family, we purpose at all times and in all places, to set apart in one's heart Jesus as Lord. (1 Peter 3:15)

- i. Calculate the values of β , I_E , R_B and R_C 7 marks
- ii. Sketch the output load-line 5 marks

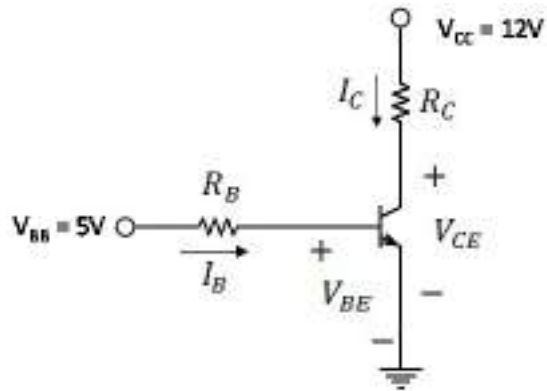


Figure 5.2



UNIVERSITY EXAMINATIONS

SECOND SEMESTER, 2018/2019 ACADEMIC YEAREXAMINATION FOR THE DEGREE OF BACHELOR OF SCIENCE INEDUCATION SCIENCE/BSC IN TELECOMMUNICATIONS/BSCCOMPUTER SCIENCEPHYS 120 BASIC ELECTRONICS

STREAM: Y1S2

TIME: 9.00-11.00 AM

EXAMINATION SESSION: JAN-APR

DATE: 10/04/2019

INSTRUCTIONS:

Answer Question 1 and any other THREE

Question 1 (30 marks)

- a) List the advantages of semiconductor devices over vacuum based devices. [4]
- b) You are given figure 1 below. Copy the diagram and label it to obtain
- a) pnp transistor [2]
- b) npn transistor [2]

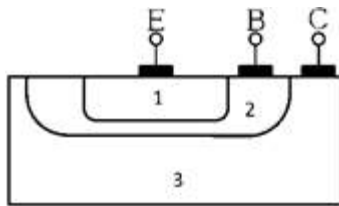


Figure 1

- c) What is the source of the leakage current in a transistor? [1]
- d) Give two examples for each of the following:
- i) donor impurity. [2]
- ii) acceptor impurity. [2]



- e) Determine the diode current at 20°C for a silicon diode with $I_s = 0.1$ A at a reverse-bias potential of 10 V. Take: Fundamental charge $q = 1.6 \times 10^{-19}$ C; Boltzmann's constant $K_B = 1.38 \times 10^{-23}$ J/K. [4]
- f) Determine α_{DC} if $I_E = 2.8$ mA and $I_B = 20 \mu\text{A}$. [3]
- g) Justify the following statements:
- "semiconductor devices can serve as source of power". [2]
 - "Semiconductor based devices saves energy" [2]
- h) In Figure 2, $V_{in} = 12$ Volts.
- Give the name of the circuit. [1]
 - Explain the operation of the circuit. [3]
 - Find voltage across AB. [2]

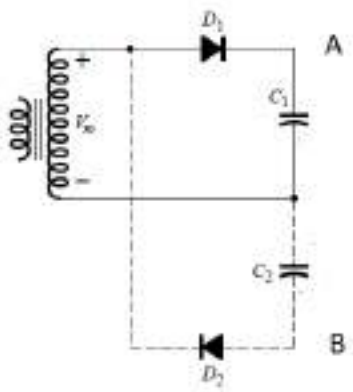


Figure 2

Question 2 (20 marks)

- Draw the 2D structure illustrating bonding Ge and explain why it is an insulator at 0K. [5]
- Describe the difference between n -type and p -type semiconductor materials. [6]
- Draw a voltage divider circuit and explain its operation. [6]
- Determine I_D , and V_o for the circuit of Fig. 3. Take the threshold of silicon to be 0.6 V. [3]

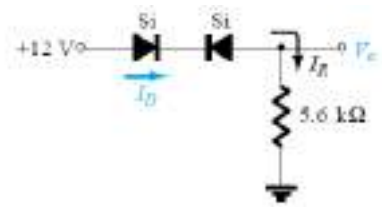


Figure 3

Question 3 (20 marks)

- a) Using the characteristics of Fig. 4: Find
- The value of I_C corresponding to $V_{BE}=750$ mV and $V_{CE}=5$ V. [2]
 - The value of V_{CE} and V_{BE} corresponding to $I_C=3$ mA and $I_B=30\mu$ A. [2]
 - The dc beta at an operating point of $V_{CE}=8$ V and $I_C=2$ mA. [3]

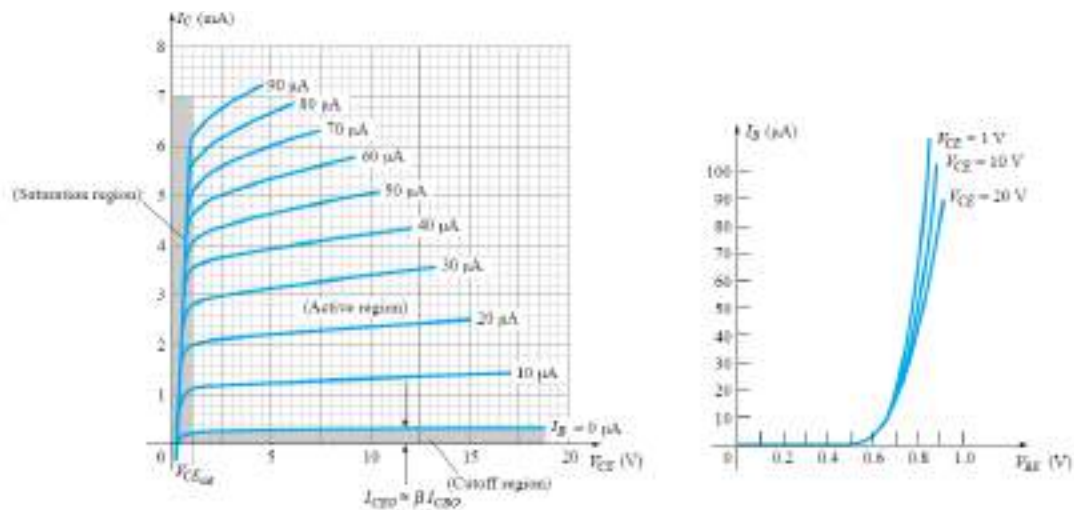


Figure 4

- Explain the desired bias condition for the three labelled operating points in Figure 4. [6]
- Determine the Q point for the circuit below (Figure 5): [7]


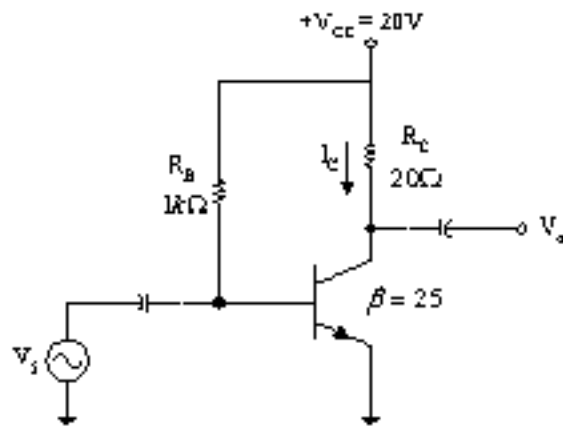


Figure 5

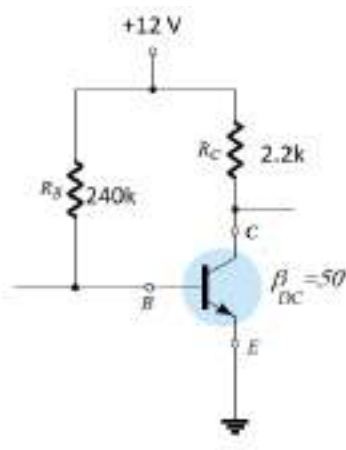Question 4 (20 marks)

- Define the Q point of a transistor circuit. [2]
- Explain factors which affect the Q point of a transistor circuit. [4]
- A Fixed Bias circuit is presented in Figure 6.
 - Show that the bias method is unstable. [5]
 - Draw its load line and mark the Q-point. (Take $V_{BE}=7\text{ V}$). [9]



Question 5 (20 marks)

- Draw a well-biased circuit -nchannel JFET and sketch the transfer curve defined by $I_{DSS}=12\text{ mA}$ and $V_P= 6\text{ V}$. [8]
- Use transistor equations to draw similarities between JFET and BJT [6]
- Derive the voltage gain of an amplifier with feedback. [6]

KABARAK



UNIVERSITY

UNIVERSITY EXAMINATIONS

MAIN CAMPUS

FIRST SEMESTER, 2017/2018 ACADEMIC YEAR

**EXAMINATION FOR THE DEGREE OF BACHELOR OF SCIENCE IN
TELECOMMUNICATION/ BACHELOR OF EDUCATION SCIENCE/
BACHELOR OF SCIENCE IN COMPUTER SCIENCE
BACHELOR OF SCIENCE IN COMPUTER FORENSIC**

PHYS 120: BASIC ELECTRONICS

STREAM: Y1S2

TIME: 9.00-11.00 AM

EXAMINATION SESSION: DECEMBER

DATE: 8/12/2017

VENUE: AUDIT

COPIES: 200

Instructions:

*Answer **Question One** and any other **Two***

- a) Draw typical band structures illustrating the band gap of:
- i. a metal, 1 point
 - ii. an insulator 1 point
 - iii. a semiconductor 1 point
- b) Describe the working of a photodiode 3 points
- c) Draw the symbols of the following:
- i. zener diode 1 points
 - ii. npn transistor 1 points
 - iii. pchannel –JFET 1 points

- d) Distinguish between a valence electron and a conduction electron 2 points
- e) Explain how BJT can be used as an amplifier. 3 points
- f) Why CE configuration is most popular in amplifier circuits? 1 point
- g) Draw the current – voltage characteristic of a Si diode for two temperatures ($T_2 > T_1$) in common coordinate system. Explain the nature of the graph. 6 points
- h) Figure 1.1 shows a battery less radio.

Radios require DC bias. Explain how the conversion from AC to DC is done (with clear diagram(s)). 5 points



Figure 1.1

- j) i. Give a circuit representing voltage divider bias 3 points
- ii. State one advantage and disadvantage of voltage divider circuit. 2 points

Question 2 (20 marks)

- a) Consider the circuit in Figure 2
 - i. State the name of the circuit. 1 point
 - ii. Find the peak secondary voltage 1 point
 - iii. Sketch the voltage waveform across R_L . 2 points
 - iv. Calculate the output DC voltage 2 points

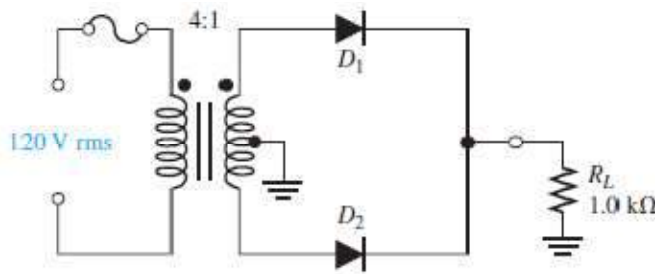


Figure 2-1

b) Discuss FOUR applications of diodes.

12 points

Question 3 (20 marks)

a) State the purpose of dc biasing circuits.

2 points

b) Explain what it means by a transistor operating in:

i. Cutoff

2 points

ii. Saturation

2 points

c) As a basic electronics student, explain why a radio receiver operating on low battery is likely to produce a distorted output.

3 points

d) In Figure 3.1, $R_B = 100k$ and $\beta = 100$.

i. Show that saturation current and cutoff voltages are as indicated on the graph.

4 points

ii. Copy the graph and mark the Q point.

7 points

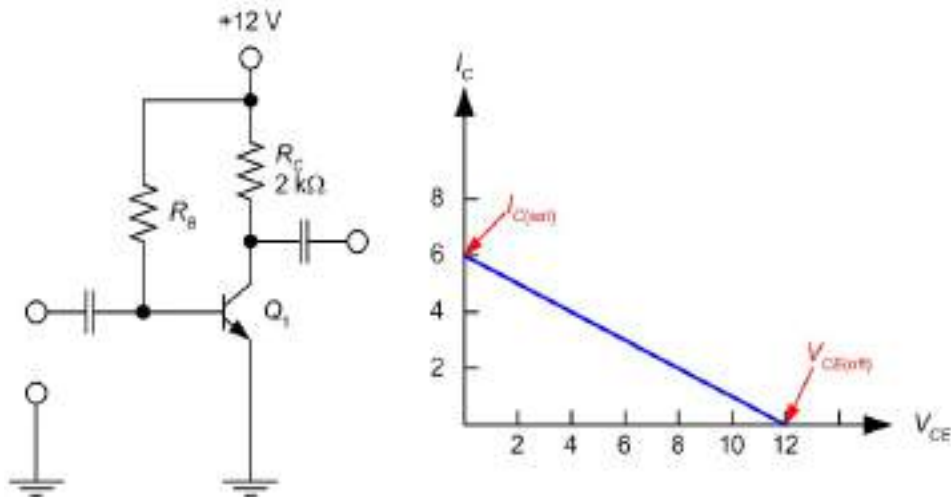


Figure 3.1

Question 4 (20 marks)

a) Using a circuit accompanied with a mathematical proof, show how an op-AMP can be used as:

a. An integrator

4 points

b. An ADDER

4 points

b) Discuss the role of dopants in a semiconductor.

3 points

c) Explain THREE methods of fabricating pn junctions.

9 points

Question 5 (20 marks)

- a) Electronics plays key role in modern computers. Identify SIX functions or parts of the computer which require electronic parts. You must state the role of the part/function you identify. 12 points
- b) Draw a well-labeled circuit representing voltage divider bias. 4 points
- c) Briefly describe the principle working of a solar cell. 4 points

KABARAK



UNIVERSITY

UNIVERSITY EXAMINATIONS

SECOND SEMESTER, 2017/2018 ACADEMIC YEAR

EXAMINATION FOR THE DEGREE OF BACHELOR OF EDUCATION (SCIENCE)

TLCM AND PHYSICS

PHYS 120 BASIC ELECTRONICS

STREAM: Y1Y2

TIME: 9.00-11.00A.M

EXAMINATION SESSION: APRIL 2018

DATE: 13/04/2018

Answer Question1 and any other two.

- a) When a transistor is used as a switch, it is stable in which two distinct regions? [2marks]
- b) Figure 1 is a voltage regulator.
 - i). Which element dictates the maximum level of source voltage? [1mark]
 - ii). Assume the input is 30 volts DC. Estimate the output. [2marks]
 - iii). Explain the operation of the circuit. [4marks]

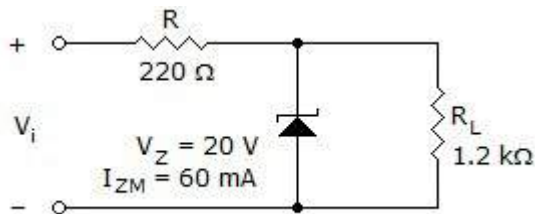


Figure 1

- c) Name any two common semiconductors. [2marks]
- d) What is the common application common collector configuration? [1mark]
- e) For Figure 2,
 - i) Give the name of the circuit [1mark]
 - ii) Determine the voltages in each capacitor. [6marks]


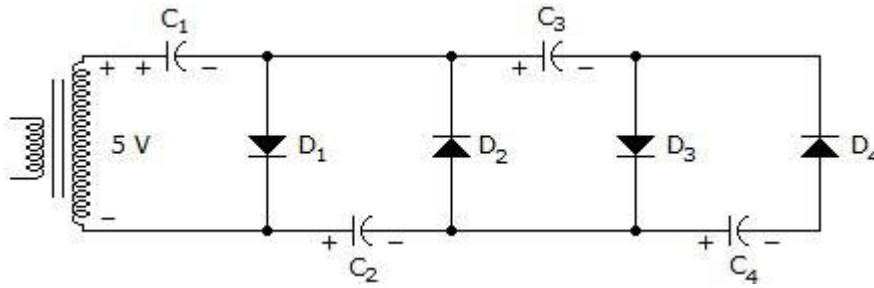


Figure 2

- f) Using a diagram, explain the operation of N channel JFET. [6marks]
 g) Explain how a p type semiconductor can be achieved. [5marks]

QUESTION 2 (20 MARKS)

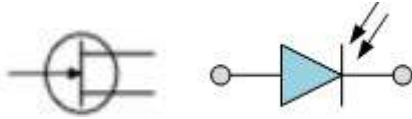- a) Explain the importance of Q point in a transistor circuit. [2marks]
 b) Give the name and role of devices represented by the following two symbols. [4marks]



- c) Refer to this Figure 4. Assuming $V_{BE} = 0.6V$,
 i). Determine V_{CE} [8marks]
 ii). draw the loadline and locate the Q point [6marks]

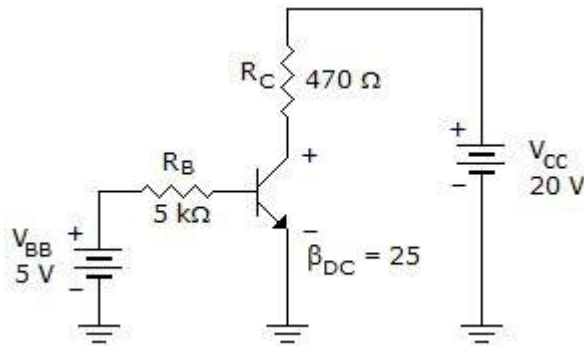


Figure 4

QUESTION 3 (20 MARKS)

- a) Refer to figure 5.
 i). Name the device [1mark]
 ii). Explain the formation of Depletion layer [3marks]
 iii). Explain the role of depletion layer in this device [3marks]
 iv). Explain the operation of the device. [7marks]

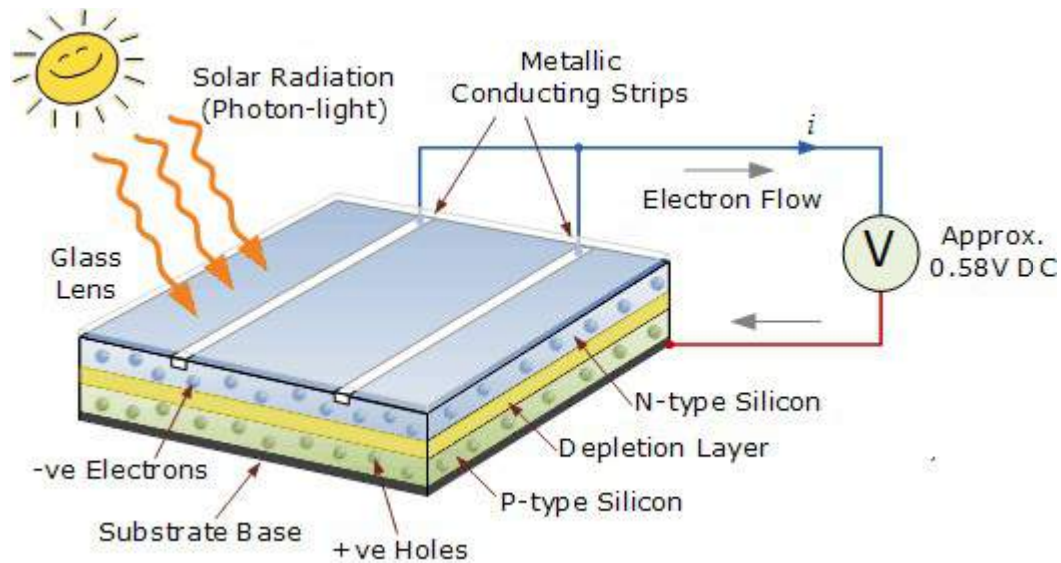


Figure 5

b) Compare FET and BJT

[6marks]

QUESTION 4 (20 MARKS)

a) Figure 3 is a circuit for lighting an LED.

i) Explain the circuit operation.

[3marks]

ii) Compute the maximum current through the LED. Assume the transistor has $V_{BE} = 0.6V$ and gain = 90.

[5marks]

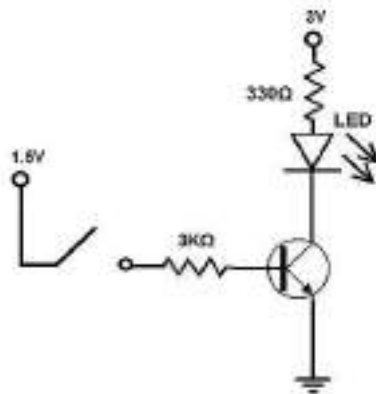


Figure 3

b) Discuss the FOUR operating modes of a transistor.

[12marks]

QUESTION 5 (20 MARKS)

a) Give any 3 characteristics of an OP AMP

[3marks]

b) Using a suitable circuit, show how an op amp can be used as an integrator

[7marks]

c) Discuss 4 advantages of negative feedback in amplifiers.

[10marks]

KABARAK



UNIVERSITY

UNIVERSITY EXAMINATIONS
MAIN CAMPUS

THIRD SEMESTER, 2016/2017 ACADEMIC YEAR

EXAMINATION FOR THE DEGREE OF BACHELOR OF SCIENCE IN
TELECOMMUNICATIONS/ BACHELOR OF SCIENCE IN EDUCATION/
BACHELOR OF SCIENCE IN COMPUTER SCIENCE

PHYS 120: BASIC ELECTRONICS

STREAM: Y1S2

TIME: 9.00-11.00AM

EXAMINATION SESSION: AUGUST

DATE: 1/08/2017

INSTRUCTIONS

- Instructions to candidates: Answer **QUESTION ONE** and any other **TWO** questions

Answer Question 1 and any other two

Question 1 (30 marks)

- | | | |
|----|---|---------|
| a) | Define a valence electron | 1 mark |
| b) | Discuss electron energy levels. | 5 marks |
| c) | Draw the symbols of npn and pnp transistor | 2 marks |
| d) | Distinguish between intrinsic and extrinsic semiconductors | 2 marks |
| e) | Describe how doping leads to the formation <i>n</i> -type semiconductor | 6 marks |
| f) | For Figure 1.1, | |
| a. | Give the name of the circuit | 1 mark |
| b. | Explain its operation. | 5 marks |
| c. | Calculate the output voltage | 3 marks |

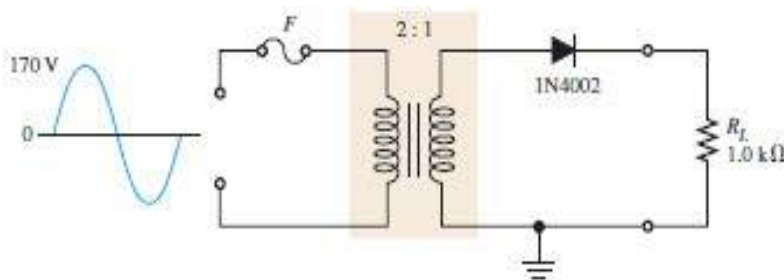


Figure 1.1

g) Explain the role of all the components in the Figure. 1.2.

5 marks

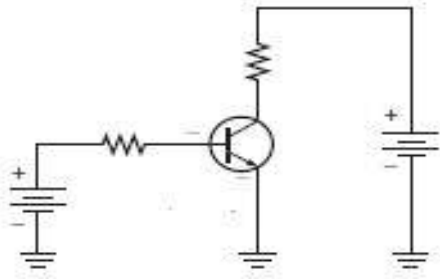


Figure 1.2

Question Two (20 marks)

- a) Using a suitable diagram, discuss bonding in semiconductors. 7 marks
- b) Why does a semiconductor have fewer free electrons than a conductor? 4 marks
- c) Describe experimentally how the diode characteristics can be determined. 9 marks

Question Three (20 marks)

- a) Discuss ANY THREE similarities between BJT and FET 6 marks
- b) Determine the dc current gain β_{DC} and the emitter current I_E for a transistor where $I_B = 50 \mu A$ and $I_C = 3.65 mA$. 4 marks
- c) Determine I_B , I_C , I_E , V_{BE} , and V_{CE} in the circuit of Figure 3.1. The transistor has a $\beta_{DC} = 150$.

10 marks

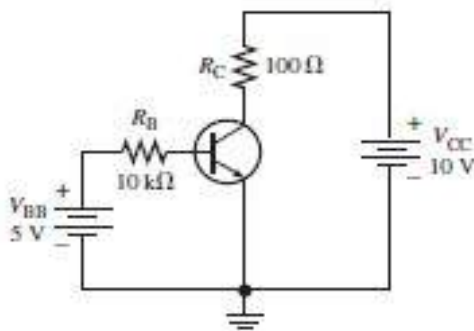


Figure 3.1

Question Four (20 marks)

- a) Discuss any two biasing methods 10 marks
- b) Highlight ANY 3 faults that can befall a transistor circuit 3 marks
- c) Figure 4.1 is a basic transistor bias circuit with all voltages referenced to ground. $\beta_{DC} = 200$. Confirm that the values displayed on meters are correct. 7 marks

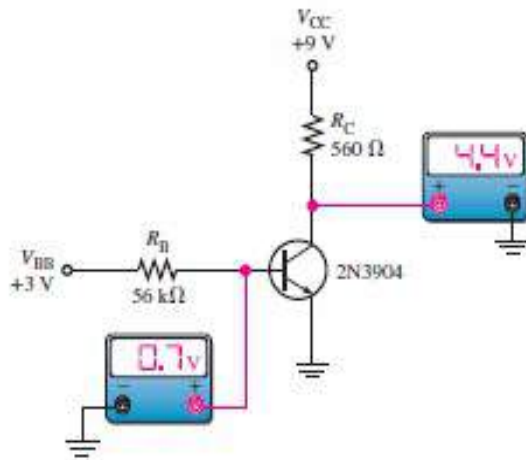


Figure 4.1

Question Five (20 marks)

- Discuss FOUR applications semiconductors
- Explain the operation modes of a transistor

12 marks

8 marks